


Problem 1;

A = 1, B = 2

Place binary output value after **EVERY** gate to trace through this logic circuit.

Place the binary answer in display.

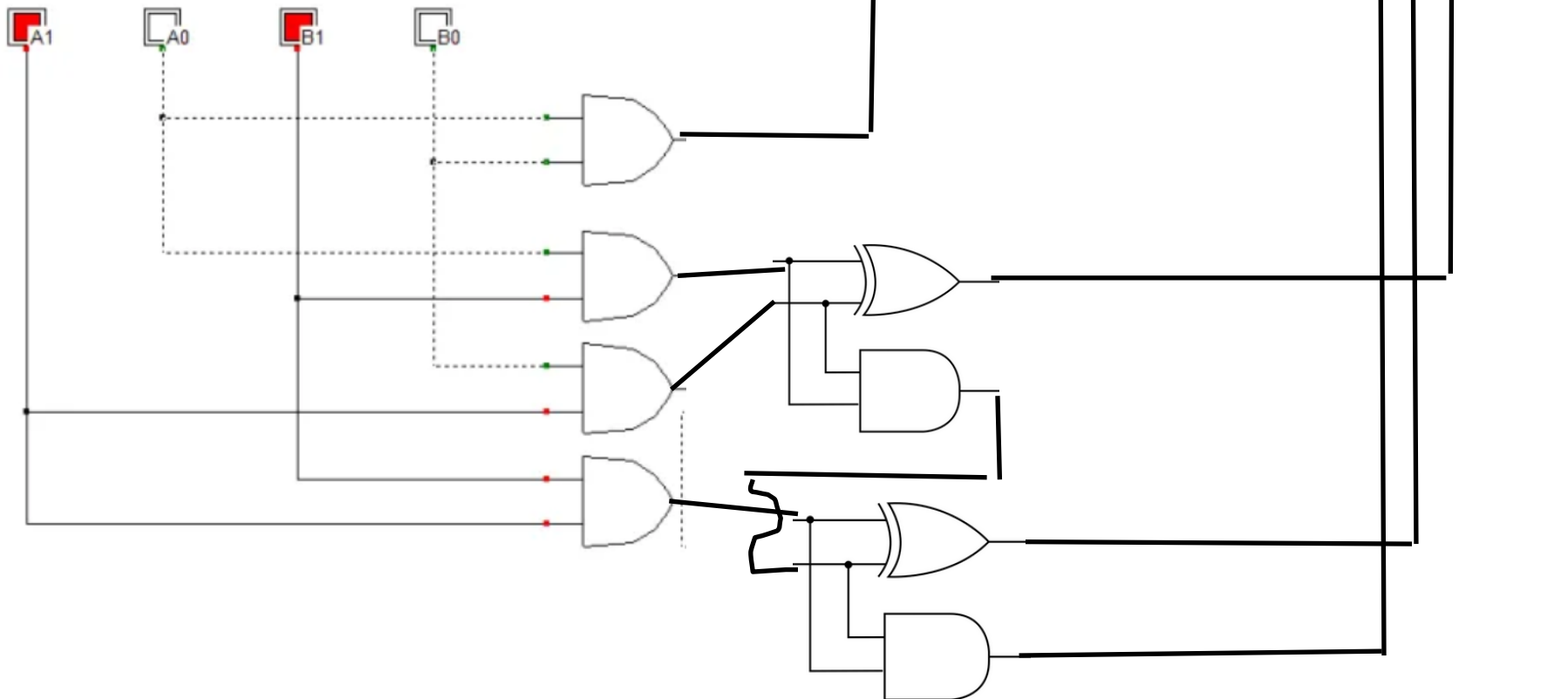What specific type of logic circuit is this?




Problem 2;

A = 7, B = 4

Place binary output value after **EVERY** gate to trace through this logic circuit.

Place binary answer in display.

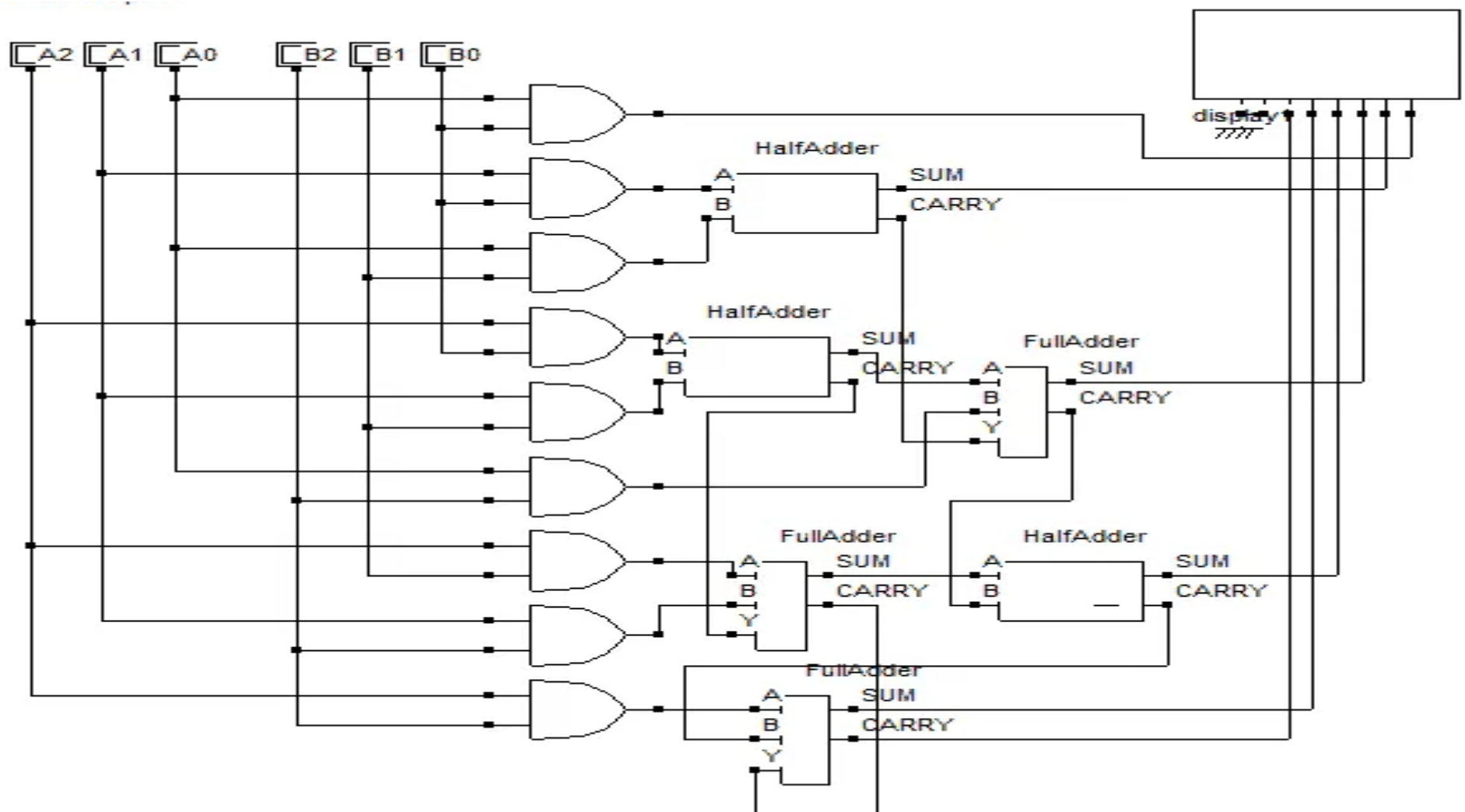What specific type of logic circuit is this? _____



Problem 3;

Build a combinational circuit for a base 4 to binary encoder AND a binary to base 4 decoder.

Create truth tables, Boolean expression for each output, and logic diagram

